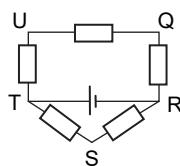





- 7.** Five resistors, each of  $50\ \Omega$ , are connected in a loop as shown below. A  $10.0\text{ V}$  battery of zero internal resistance is connected across TR. What is the potential difference between U and R,  $V_{UR}$ ?




- (A)  $10.0\text{ V}$       (B)  $8.7\text{ V}$   
 (C)  $6.7\text{ V}$       (D)  $3.7\text{ V}$

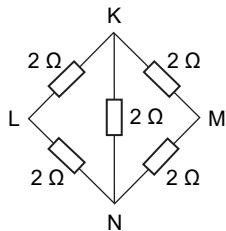- 8.** What is the equivalent resistance between the terminals L and M in the circuit below?




- (A)  $1\ \Omega$       (B)  $2\ \Omega$   
 (C)  $3\ \Omega$       (D)  $4\ \Omega$

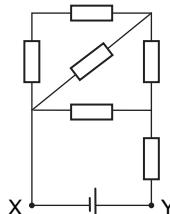- 9.** The resistance of each resistor in the circuit is  $R$ . What is the effective resistance across XY?



- (A)  $\frac{R}{2}$       (B)  $\frac{2R}{3}$   
 (C)  $\frac{13R}{8}$       (D)  $\frac{18R}{3}$





**10.**

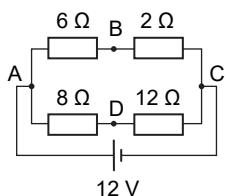

The value of the potential difference across BD is

- (A)  $3.2\text{ V}$       (B)  $-4.8\text{ V}$   
 (C)  $-4.2\text{ V}$       (D)  $5.0\text{ V}$

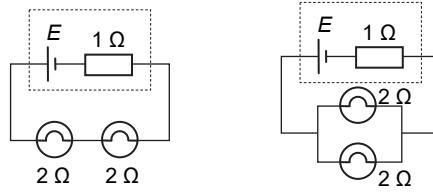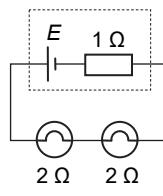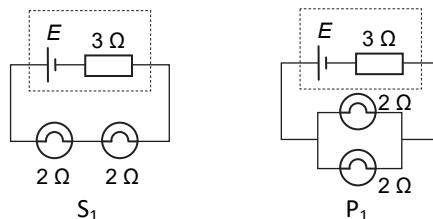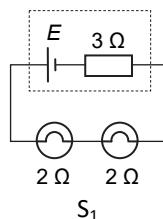
- 11.** Cells that have the same e.m.f. E but different internal resistances are used to power two lamps, either connected in series or parallel, as shown in the figures below. Each lamp may be considered to have a constant resistance of  $2\ \Omega$ .



Which of the following gives the combinations in order of decreasing light output?

- (A)  $P_2, S_2, S_1, P_1$       (B)  $P_1, S_1, S_2, P_2$   
 (C)  $P_2, P_1, S_2, S_1$       (D)  $S_1, S_2, P_1, P_2$

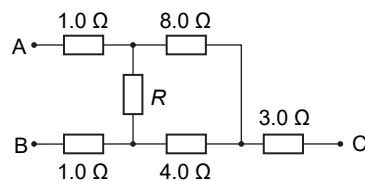- 12.** The diagram shows a network of six resistors. The resistance between A and C is  $8.0\ \Omega$ . What is the value of resistance  $R$ ?



- (A)  $1.0\ \Omega$       (B)  $4.0\ \Omega$   
 (C)  $6.0\ \Omega$       (D)  $8.0\ \Omega$